

Introduction to Verilog

Review on Digital Logic Design

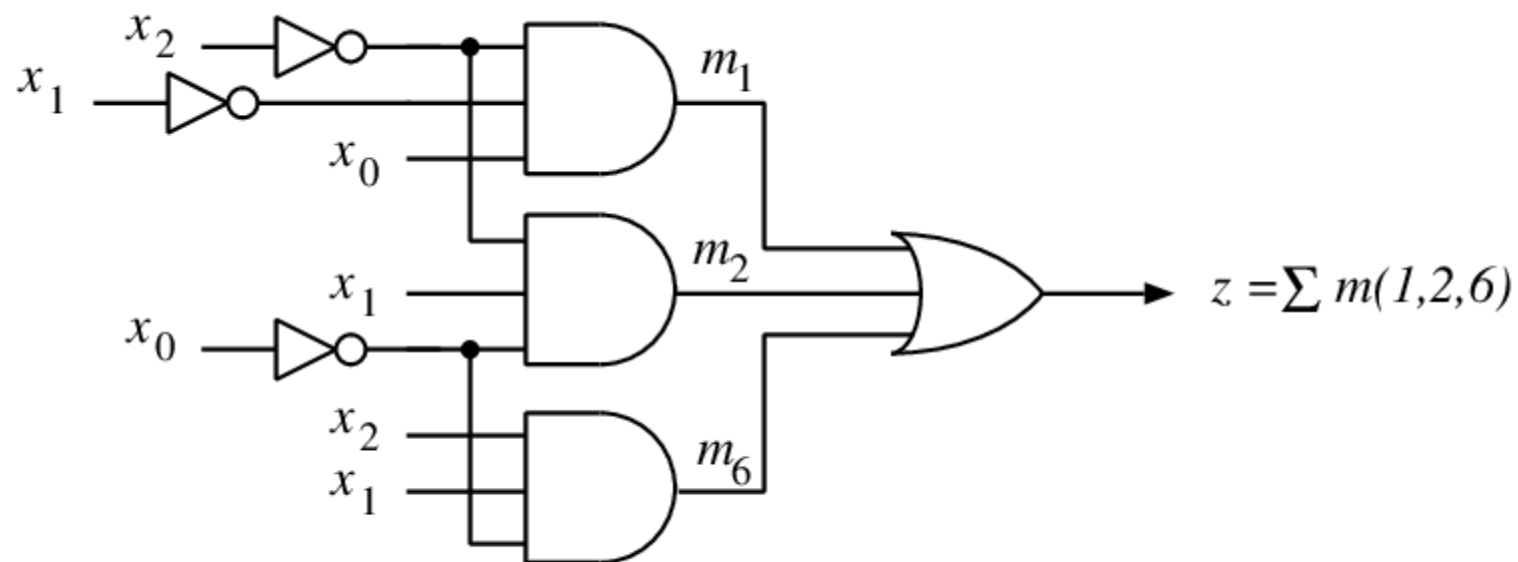


Figure 2.8: Gate network corresponding to $E(x_2, x_1, x_0) = \sum m(1, 2, 6)$.


 
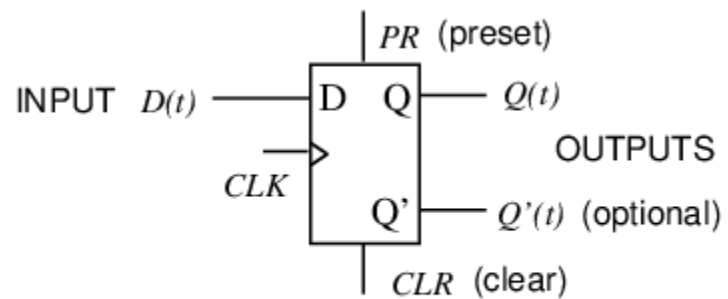


Figure 8.12: D flip-flop and its state diagram.

 


 
 


Figure 8.12: D flip-flop and its state diagram.

 

Input: $x(t) \in \{a, b, c\}$
 Output: $z(t) \in \{0, 1\}$
 State: $s(t) \in \{A, B, C, D\}$
 Initial state: $s(0) = A$

Functions: The state-transition and output functions

PS	Input		
	$x = a$	$x = b$	$x = c$
A	$C, 0$	$B, 1$	$B, 0$
B	$D, 0$	$B, 0$	$A, 1$
C	$A, 0$	$D, 1$	$D, 0$
D	$B, 0$	$A, 0$	$D, 1$
	NS, z		

Coding:

Input code		
x	x_1	x_0
a	0	1
b	1	0
c	1	1

State code		
s	y_1	y_0
A	0	0
B	1	0
C	0	1
D	1	1

- State-transition and output functions

PS	x_1x_0		
y_1y_0	01	10	11
00	01,0	10,1	10,0
10	11,0	10,0	00,1
01	00,0	11,1	11,0
11	10,0	00,0	11,1
	Y_1Y_0, z		
	$NS, \text{ Output}$		

$Y_1:$

	x_0			
y_1				y_0
	x_1			

- State-transition and output functions

PS	x_1x_0		
y_1y_0	01	10	11
00	01,0	10,1	10,0
10	11,0	10,0	00,1
01	00,0	11,1	11,0
11	10,0	00,0	11,1
	Y_1Y_0, z		
	$NS, \text{ Output}$		

$$Y_1:$$

		x_0	
-	0	1	1
-	0	1	1
-	1	1	0
-	1	0	1
		x_1	

$$y_1 \left| \begin{array}{c} \text{table} \end{array} \right| y_0$$

- State-transition and output functions

PS	x_1x_0		
y_1y_0	01	10	11
00	01,0	10,1	10,0
10	11,0	10,0	00,1
01	00,0	11,1	11,0
11	10,0	00,0	11,1
	Y_1Y_0, z		
	$NS, \text{ Output}$		

$$Y_1: \begin{array}{c|cc|c} & \overbrace{\quad x_0 \quad} & & \\ & - & 0 & 1 & 1 \\ & - & 0 & 1 & 1 \\ y_1 & - & 1 & 1 & 0 \\ & - & 1 & 0 & 1 \\ & \underbrace{\quad x_1 \quad} & & \end{array} \Bigg| y_0$$

$$Y_1 = y_1'x_1 + y_1x_1' + y_0'x_0' + y_0x_1x_0$$

- State-transition and output functions

PS	x_1x_0		
y_1y_0	01	10	11
00	01,0	10,1	10,0
10	11,0	10,0	00,1
01	00,0	11,1	11,0
11	10,0	00,0	11,1
	Y_1Y_0, z		
	$NS, \text{ Output}$		

$$Y_1: \begin{array}{c|ccc} & \overbrace{x_0} & & \\ & - & 0 & 1 & 1 \\ y_1 & - & 0 & 1 & 1 \\ & - & 1 & 1 & 0 \\ & - & 1 & 0 & 1 \\ & \underbrace{x_1} & & & \end{array} \Bigg| y_0$$

$$Y_0: \begin{array}{c|ccc} & \overbrace{x_0} & & \\ & - & 1 & 0 & 0 \\ y_1 & - & 0 & 1 & 1 \\ & - & 0 & 1 & 0 \\ & - & 1 & 0 & 0 \\ & \underbrace{x_1} & & & \end{array} \Bigg| y_0$$

$$z: \begin{array}{c|ccc} & \overbrace{x_0} & & \\ & - & 0 & 0 & 1 \\ y_1 & - & 0 & 0 & 1 \\ & - & 0 & 1 & 0 \\ & - & 0 & 1 & 0 \\ & \underbrace{x_1} & & & \end{array} \Bigg| y_0$$

$$Y_1 = y_1'x_1 + y_1x_1' + y_0'x_0' + y_0x_1x_0$$

$$Y_0 = y_0'x_1' + y_1'y_0x_1 + y_0x_1x_0$$

$$z = y_1'x_0' + y_1x_1x_0$$

 


Figure 8.19: Sequential network in Example 8.4.

 


Figure 8.19: Sequential network in Example 8.4.

Verilog

Introduction to Verilog

Overview of Verilog

1. Resemblance to C: case sensitive, same style comments, operators, etc.
2. Two standards: Verilog-1995, Verilog-2001, both supported by ISE
3. VHDL is the other widely used HDL.

Behavioral vs Synthesizable code


Historically Verilog has always served two functions:

1. Describe your digital logic design in a high-level way instead of using schematics (synthesizable code).
2. Model elements that interact with your design (behavioral models/testbenches)

You should **always** have a clear conscience of whether you are writing behavioral or synthesizable code.

Better yet, know what your synthesizable code translates to in **physical hardware**.

Behavioral vs Synthesizable code

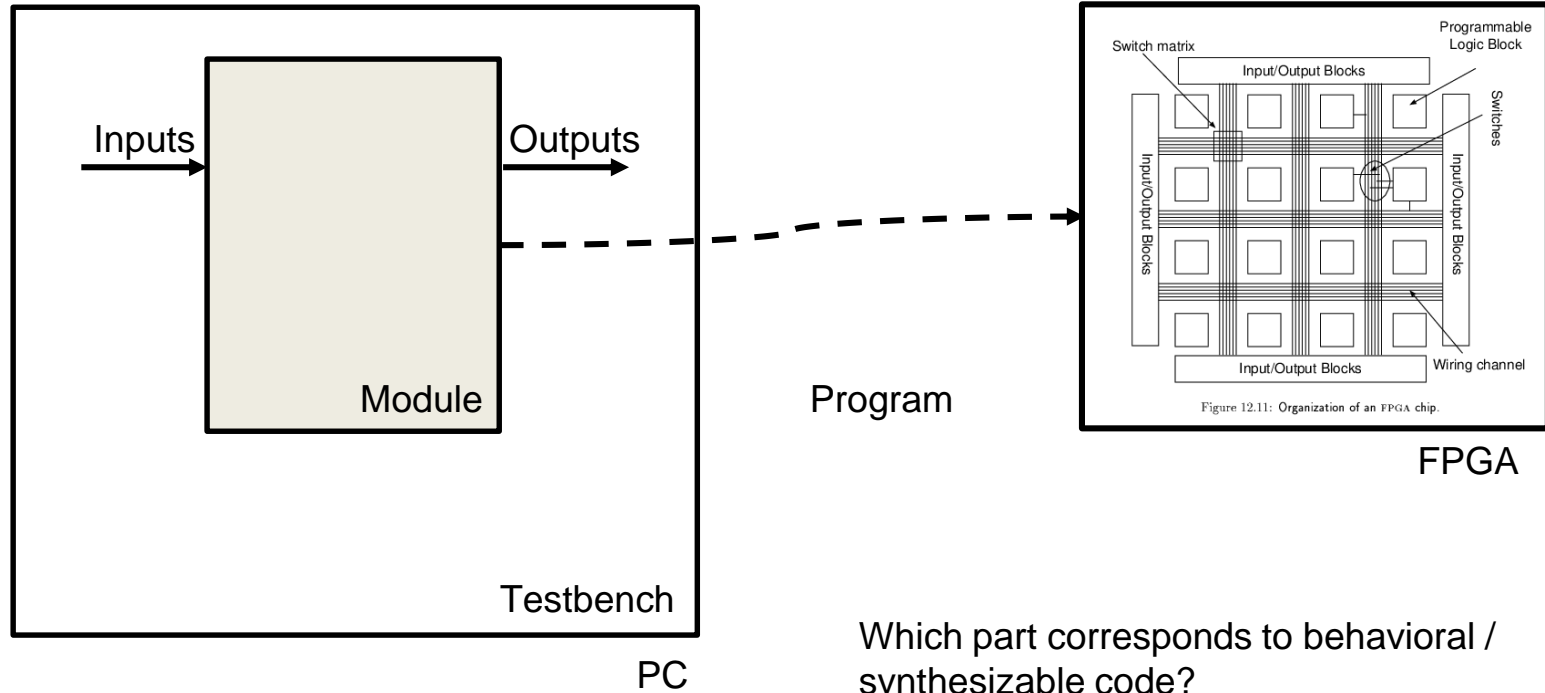

Data types: wire, reg

Variables must be declared before used; wire/reg are the most common data types.

wire:

- models basic wire that holds transient values

reg:

- anything that stores a value

Data Values

Values: 1, 0, x/X (unknown), z/Z (high impedance)

Radices: d(decimal), h(hex), o(octal), b(binary)

Format: <size>'<radix><value>

123 // default: decimal radix, unspecified width

'd123 // 'd = decimal radix

8'h7B // 'h = hex radix

'o173 // 'o = octal radix

'b111_1011 // 'b = binary radix, "_" are for readability

Signed number (rarely used):

8'shFF (8-bit twos-complement representation of -1)

Operators

Bitwise: $\sim a$, $a \& b$, $a | b$, $a \wedge b$, $a \sim \wedge b$

Reduction: bitwise operation on a **single** operand and produces one bit result.

$\&a$, $\sim \&a$, $|a$, $\sim |a$, $\wedge a$, $\sim \wedge a$

Example: $\wedge 4'b1001 = 1'b0$

Logical: output one bit result

$!a$, $a \&\&b$, $a || b$, $==/!=$, $===/!==$ (also compares x/z)

Arithmetic: $+$, $-$, $*$, $/$, $\%$ (mod, takes the sign of operand 1)

Operators, ctd.

Can you tell the difference between the following expressions? What are the sizes of each expression and what do they mean?

Declaration: wire [31:0] a,b

- `a & b`
- `a && b`
- `(&a) & (&b)`
- `(&a) && (&b)`
- `&(a && b)`
- `a && (&b)`

Operators, ctd.

Shift: <<, >>(logical)
 <<<, >>> (arithmetic)

Conditional: sel ? a : b

Concatenation: {a, b}

Replication: {n{m}}

Assignment: =(blocking), <= (non-blocking)

Blocking/Non-blocking assignments

Blocking assignments (=):

assignment immediate, happens first

Non-blocking assignment(<=):

assignments deferred until all right hand sides has been evaluated, closer to actual hardware register behavior.

Assignment operator guidelines

1. Sequential logic: use nonblocking (\leq)
2. Pure combinational logic in “always” block: use blocking ($=$)
3. Do not mix blocking/non-blocking in the same “always” block
4. Both sequential and “combinational” logic in the same “always” block: use non-blocking (\leq)

`y <= a ^ b;`

Recommendation: in complex sequential circuit, use two always blocks, one for combinational circuit, one for state update.

Basic building block: modules

1. port: input / output / inout
2. Signal declarations: `wire [3:0]`
`a;`
 - a. Rule-of-thumb: stick to [MSB:LSB]
3. Concurrent logic blocks, one of the following:
 - a. continuous assignments
 - b. always blocks (either sequential or combinatorial)
 - c. initial blocks (only used in behavioral modeling)
 - d. forever blocks (only used in behavioral modeling)
4. Instantiations of sub-modules

```
module top(a, b, ci, s, co
    );
    input a, b, ci;
    output s, co;

    wire s;
    reg g, p, co;

    assign s = a ^ b ^ ci;
    // combinatorial always
    // block using begin/end
    always @* begin
        g = a & b;
        p = a | b;
        co = g | (p & ci);
    end

endmodule
```


Basic building block: modules

1. port: input / output / inout
2. Signal declarations: `wire [3:0]`
`a;`
 - a. Rule-of-thumb: stick to [MSB:LSB]
3. Concurrent logic blocks, one of the following:
 - a. continuous assignments
 - b. always blocks (either sequential or combinatorial)
 - c. initial blocks (only used in behavioral modeling)
 - d. forever blocks (only used in behavioral modeling)
4. Instantiations of sub-modules

```
module top(a, b, ci, s, co
    );
    input a, b, ci;
    output s, co;

    wire s;
    reg g, p, co;

    assign s = a ^ b ^ ci;
    // combinatorial always
    // block using begin/end
    always @* begin
        g = a & b;
        p = a | b;
        co = g | (p & ci);
    end

endmodule
```

Always Block

```
// combinatorial always  
// block using begin/end  
always [*] begin  
    g = a & b;  
    p = a | b;  
    co = g | (p & ci);  
end
```

Sensitivity list

Code that describes the real
“function”

Always Block: Sensitivity list

1. Level sensitive: changes to any signals on the sensitivity list will invoke the always block. Used in combinational circuits.

`always @ (a or b) / always @* (verilog-2001, recommended)`

1. Edge sensitive: invoke always block on specified signal edges. Used in sequential circuits.

`always @ (posedge clk or posedge reset)`

Aways Block: case, if/else

```
case (sel)
  val0: statements
  val1: statements
  ...
  default: statements
endcase
```

```
if (condition)
  statements
else if (condition)
  statements
...
else
  statements
```

Aways Blocks: case, if/else ctd.

```
module ALU(a, b, f, z
);
input [3:0] a, b;
input [1:0] f;
output reg [3:0] z;

always @(*)
    z = 4'bx; (#1)
    case (f)
        0: z = a + b;
        1: z = a * b;
        2: z = a & b;
        3: z = a | b;
        default: z = 4'bx; (#2)
    endcase
endmodule
```

if/else or case statement fails to
cover all cases → **inferred latch**

Example:

```
if (x == 2'b00)
    z = a;
else if (x == 2'b01)
    z = b;
```

What about other cases? The circuit
will hold previous value
To avoid: add #1 or #2

Always Block: Looping (mostly for testing)

while (condition)
 statements

for (initialization; condition; increment)
 statements

repeat (n)
 statements

Data types: wire, reg

Variables must be declared before used; wire/reg are the most common data types.

wire:

- models basic wire that holds transient values
- **only wires can be used on the LHS of continuous assign statement**
- input/output port signals default to wire

reg:

- anything that stores a value
- can appear in both combinational and sequential circuits
- **only regs can be used on the LHS of non-continuous assign statement**

Wire vs. reg

When to use wire:

Left hand side of “assign”

```
wire s;
```

```
assign s = a ^ b ^ ci;
```

When to use reg:

Left hand side of “=” or “<=” in
“always” blocks

```
reg g, p, co;
```

```
always @* begin
```

```
    g = a & b;
```

```
    p = a | b;
```

```
    co = g | (p & ci);
```

```
end
```


Sequential circuit example: modulo 64 counter

```
module counter(clk, rst, out
);
  input clk, rst;
  output [5:0] out;

  reg [5:0] out;
  always @(posedge clk or posedge rst)
  begin
    if (rst)
      out <= 6'b000000;
    else
      out <= out + 1;
  end
endmodule
```

Module instantiation

Achieve hierarchical design by using other modules inside one module.

Recommended format:

```
type name (.port1(w1),.port2(w2).....);
```

1. Port order doesn't matter
2. Unused output port allowed
3. Name must be unique within module

Example


```
module half_adder(a, b, x, y
);
  input a, b;
  output x, y;

  assign x = a & b;
  assign y = a ^ b;
endmodule
```

```
module full_adder(a, b, ci, s, co
);
  input a, b, ci;
  output s, co;
  wire g, p, pc;

  half_adder h1(.a(a), .b(b),
    .x(g), .y(p));
  half_adder h2(.a(p), .b(ci),
    .x(pc), .y(s));
  assign co = pc | g;
endmodule
```

Schematics output

 

Testbench

Testing is important and engineers spend more time testing for complex digital circuits.

Procedures for creating testbench:

1. Instantiate unit under test (uut)
2. Provide input for uut: clk, rst, data...
3. Simulate and verify behavior

Initial block

```
initial begin
    // Initialize Inputs
    clk = 0;
    rst = 0;
    // Wait 100 ns for global reset
    to finish
    #100;
    // Add stimulus here
    rst = 1;
    #20 rst = 0;
    // add verification routine here
    #1000 $finish;
end
```

Initial block starts execution at time 0.

#n : wait n time units

\$finish: stop simulation

Parameter

```
module ALU #(parameter W=4) (a, b, f, z);  
  input [W-1:0] a, b;  
  input [1:0] f;  
  output reg [W-1:0] z;  
  
  always @(*)  
    case (f)  
      0: z = a + b;  
      1: z = a * b;  
      2: z = a & b;  
      3: z = a | b;  
      default: z = {(W){1'b0}};  
    endcase  
endmodule
```

Instantiation of Parameterized Module:

Default parameter W=4. Instantiate a 16-bit ALU:

Format:

type #(params) name (ports);

Example:

```
ALU #(.W(16)) alu16 (.a(a), .b(b), .f(f), .z(z));
```


Preparation Tasks

- Read *An Old Tutorial* on the course web
 - *Ignore the device parameters for Spartan-3*
 - *Ignore contents beyond **Create Timing Constraints***
- Create projects, write code and simulate:
 - 2:1 mux
 - `mux2(input din0, din1, sel, output out);`
 - 8 bit counter
 - `counter(output [7:0] out, input clk, ena, rst);`
 - 16-4 encoder
 - `encoder (input [15:0] in, input enable, output [3:0] out);`

References

1. MIT 6.111 course notes,
<http://web.mit.edu/6.111/www/f2013/index.html>
2. Verilog in one day,
http://www.asic-world.com/verilog/verilog_one_day.html
3. Wire vs. Reg,
<http://inst.eecs.berkeley.edu/~cs150/Documents/Nets.pdf>
4. Sunburst Design (Read on assignment operators)
<http://www.sunburst-design.com/papers/>
5. ISE Quick Start Guide
<http://cseweb.ucsd.edu/classes/wi11/cse141L/Media/Quick-Tutorial-11.pdf>